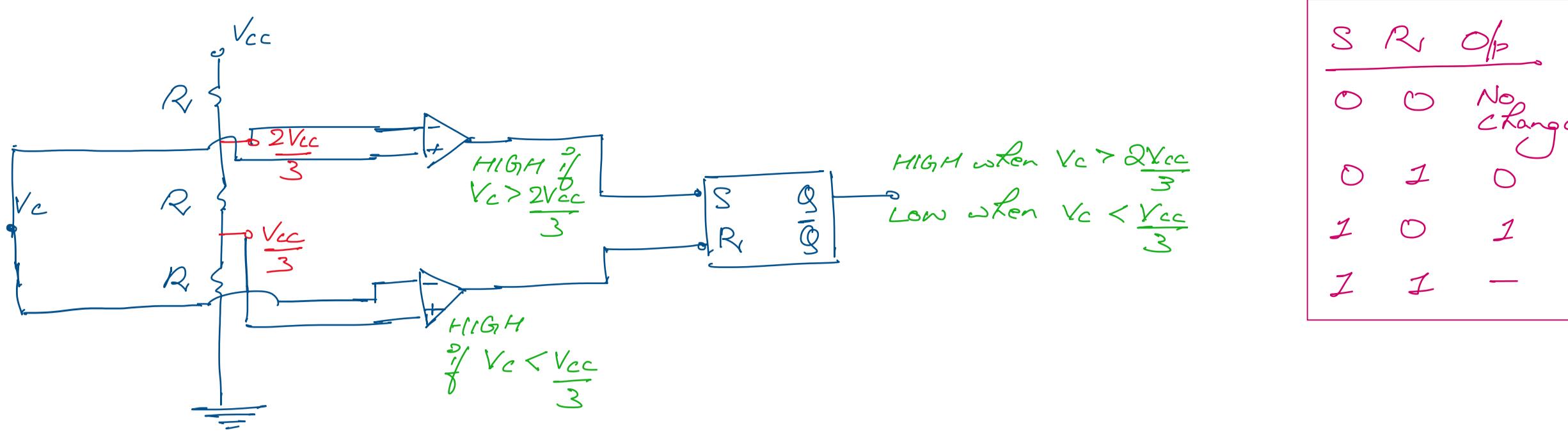


→ It can be used as an oscillator circuit. We can generate a square wave using this circuit.



→ It is made of 2 comparators & a potential divider



→ The task of the 2 comparators is to compare another voltage V_c against the two levels: $\frac{V_{cc}}{3}$ & $\frac{2V_{cc}}{3}$. That's why we have 2 comparators.

→ What I essentially want is an oscillating voltage. So the voltage will change with time.

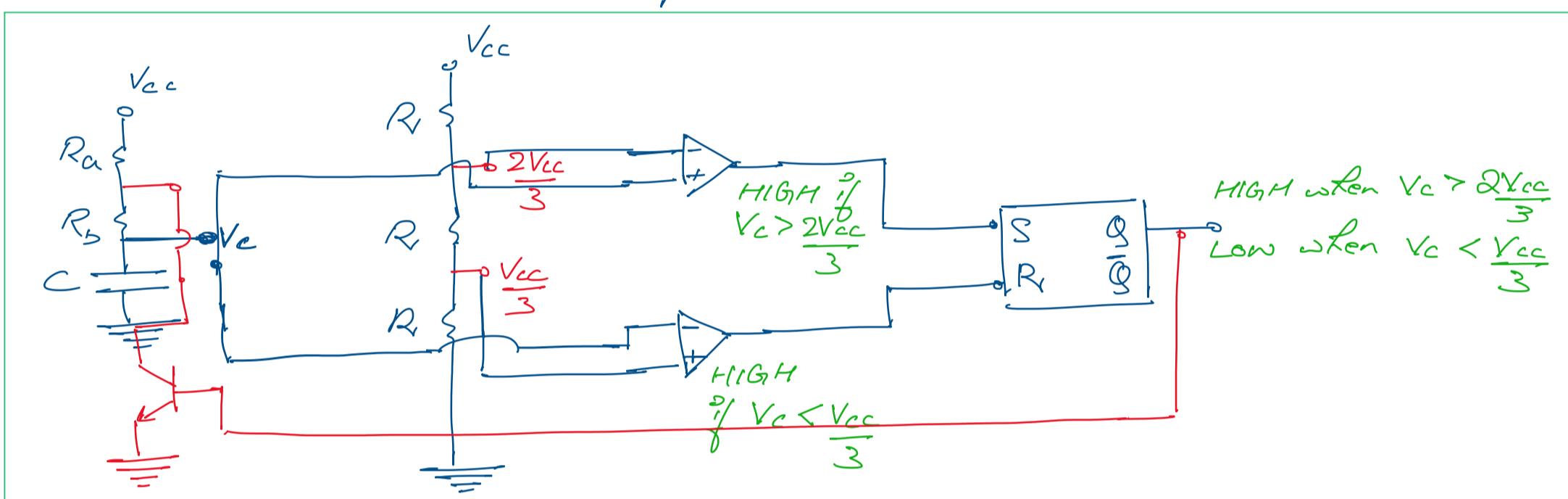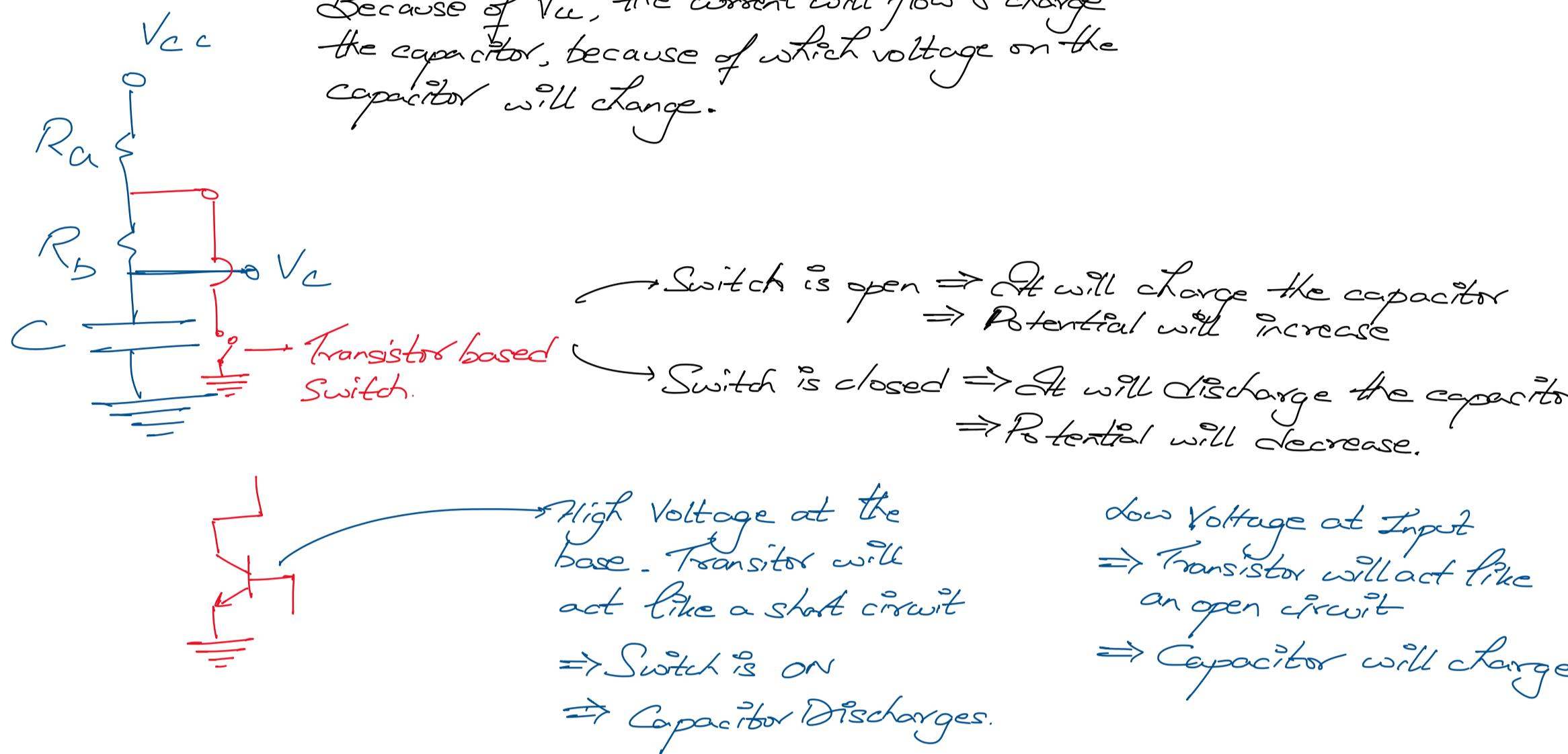Because of V_{cc} , the current will flow & charge the capacitor, because of which voltage on the capacitor will change.




Working

- ① Suppose the transistor is an open circuit.
- ② Capacitor will charge. After some time $V_c > \frac{2V_{cc}}{3}$.
- ③ Output becomes High.
- ④ Transistor shorts.
- ⑤ Capacitor starts discharging. After some time $V_c < \frac{V_{cc}}{3}$.
- ⑥ Output becomes Low.
- ⑦ Transistor again becomes open. In this way, it oscillates between charging & discharging.



$$\text{Note:- Duty Cycle} = \frac{T_{on}}{T_{on} + T_{off}}$$

Q) What is the frequency of the circuit?

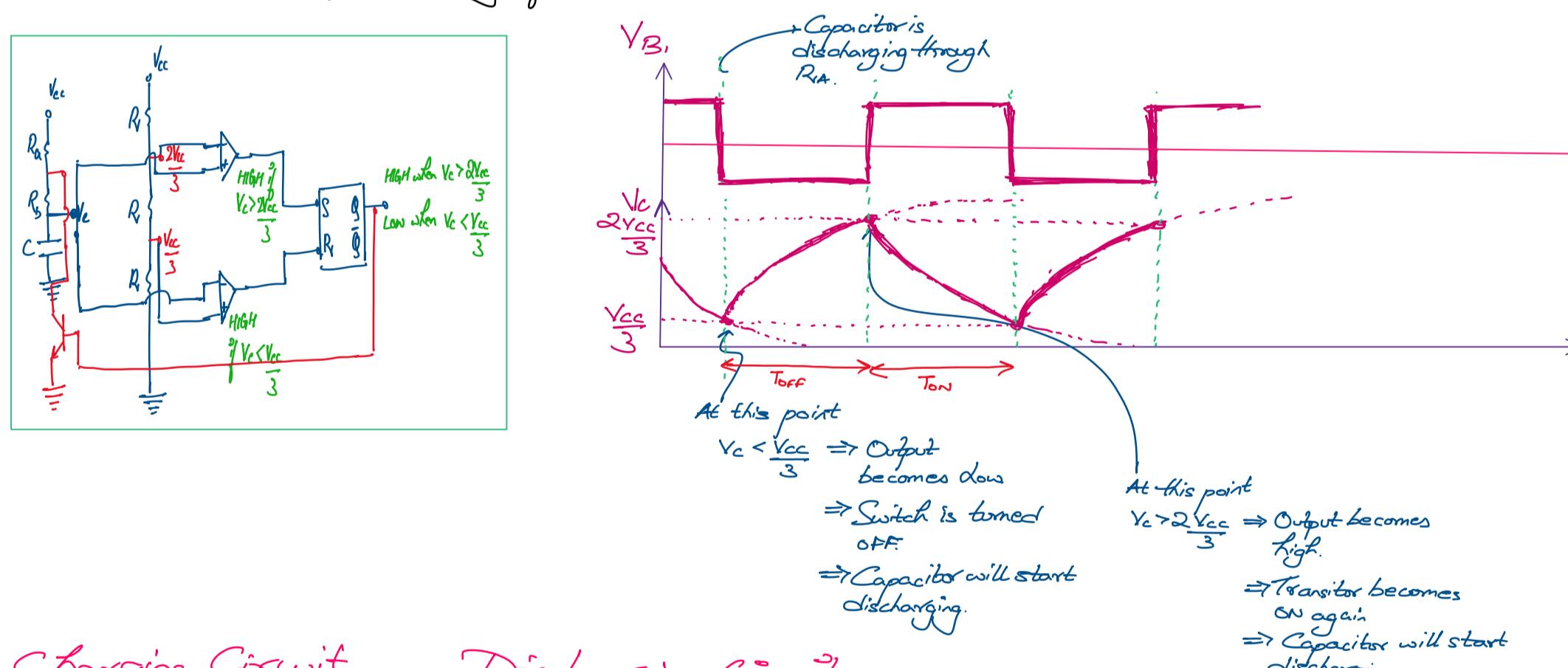

Charging Circuit

Discharging Circuit

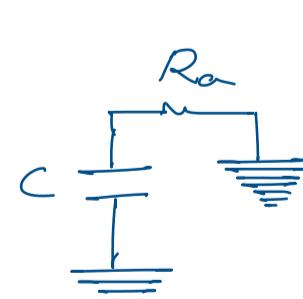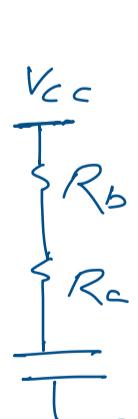

T_{off}
→ V_c starts from $\frac{V_{cc}}{3}$ & trying to go to V_{cc} .

→ Gap = Target - Initial

$$= \frac{2V_{cc}}{3}$$

$$\rightarrow V_c(t) = \text{Target} - (\text{Target} - \text{Initial}) e^{-t/\tau} \quad \text{Derived from writing the differential equation.}$$

$$\Rightarrow V_c(t) = V_{cc} - \frac{2V_{cc}}{3} e^{-t/\tau} ; \tau = (R_a + R_b)C$$

$$\Rightarrow \frac{dV_c}{dt} = V_{cc} - \frac{2V_{cc}}{3} e^{-t/\tau} \quad \text{Charging time constant.}$$

$$\Rightarrow e^{-t/\tau} = \frac{1}{2}$$

$$\Rightarrow \frac{t}{\tau} = \ln 2$$

$$\Rightarrow \tau = \frac{t}{\ln 2}$$

$$\Rightarrow T_{off} = (R_a + R_b)C \cdot \ln 2$$

T_{on}

→ V_c starts from $\frac{2V_{cc}}{3}$ & target voltage = 0V

$$\rightarrow V_c(t) = \text{Target} - (\text{Target} - \text{Initial}) e^{-t/\tau}$$

$$\rightarrow V_c(t) = \frac{2V_{cc}}{3} e^{-t/\tau} ; \tau = R_b C$$

Discharging time constant?

$$\rightarrow \frac{V_c}{V_{cc}} = \frac{2V_{cc}}{3} e^{-t/\tau}$$

$$\Rightarrow e^{-t/\tau} = \frac{1}{2}$$

$$\Rightarrow t_{on} = \tau \ln 2$$

$$\Rightarrow t_{on} = R_b C \ln 2$$

$$\text{Total Time Period} = T_{on} + T_{off}$$

$$= (R_a C \ln 2) + (R_a + R_b)C \ln 2$$