
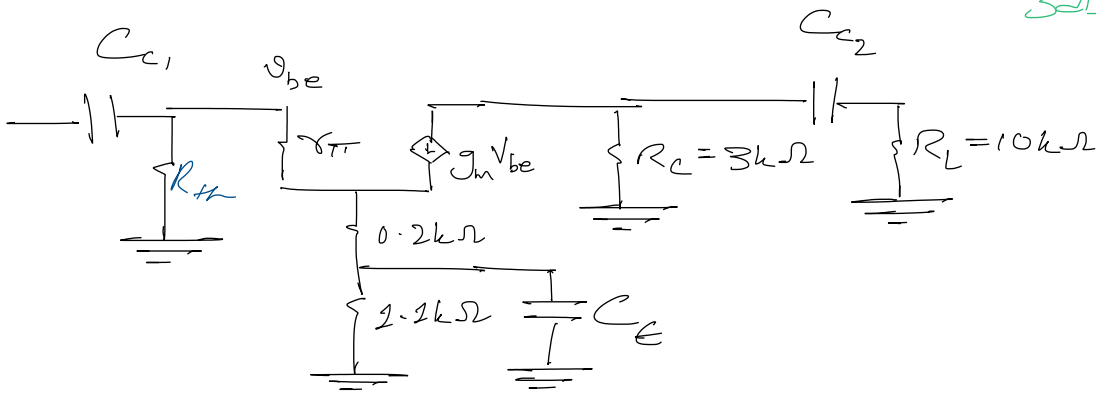
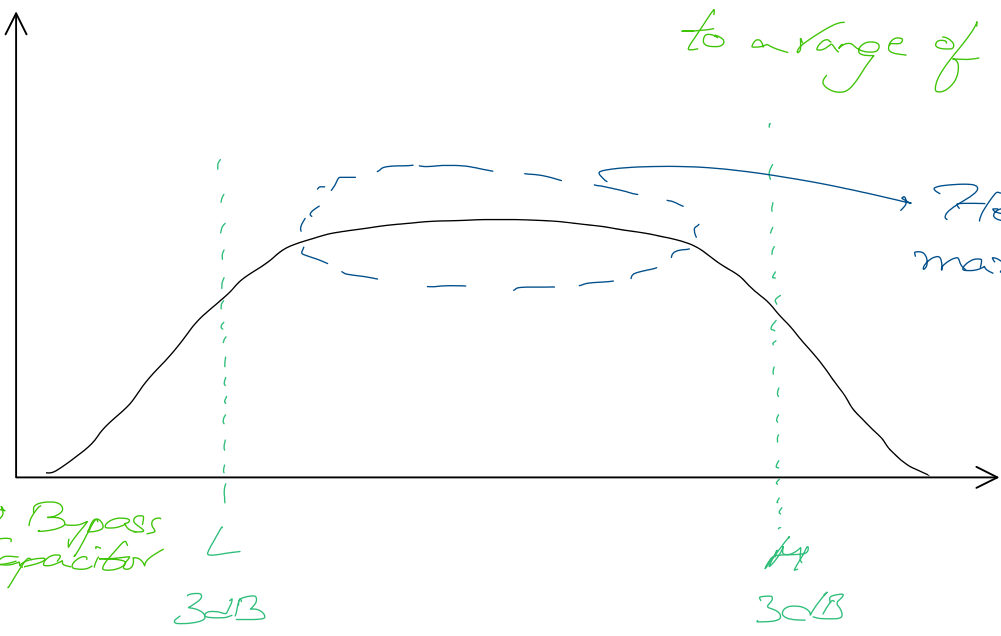


Lab 9

Thursday, 11 April 2024 1:34 PM

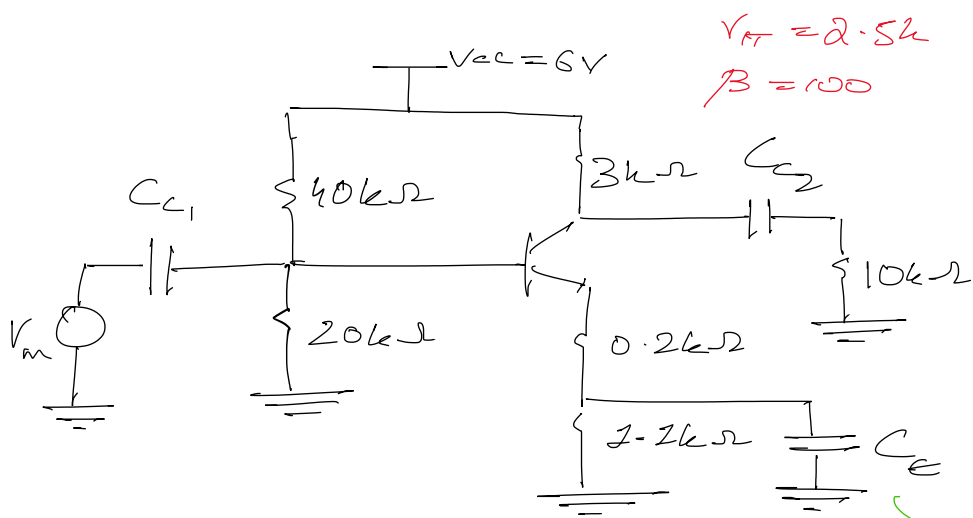

- How will a ckt respond to a range of f frequency?
- Here gain is maximum. (for this frequency response)
- low & High cutoff frequency.
- * Generally ckt operate in a band of frequency.
- * There is a low & High frequency.

$f_H|_{3dB}$ → Associated with low Capacitance
 $f_L|_{3dB}$ → Associated with High Capacitance.

* We can't control $f_H|_{3dB}$ as that is determined by internal capacitance. $\Rightarrow f_H|_{3dB} = \text{fixed}$.
What I can change is $f_L|_{3dB}$ → Depends on the 3 capacitances

- We are trying to design f_L .
- C_{c1} → will block DC & will pass only AC. → It will ensure that the DC operating point of our circuit does not shift.
- C_{c2} will remove the DC offset.

Associate an equivalent RC circuit for each capacitance so that they make a contribution in f_L .

- $R_{C_{c1}} \rightarrow C_{c1}$ } Resistance seen from capacitance terminal.
- $R_{C_{c2}} \rightarrow C_{c2}$ } Make all possible sources 0.
- $R_{C_{CE}} \rightarrow C_{CE}$ } Short circuit the capacitance.

$$R_{C_{c1}} = R_{th} || (\gamma_{\pi} + (\beta + 1)R_E)$$

$$\frac{1}{2\pi R_{C_{c1}} * C_{c1}} \rightarrow \text{gives one component of } f_L$$

- Here I can change C_{c1} .
- $R_{C_{c1}}$ is basically fixed as we don't want to disrupt DC operating point or gain.

$$R_E = R_E || R_{C1} + \frac{\gamma_{\pi}}{\beta + 1}$$

$$\frac{1}{2\pi R_E * C_E} \rightarrow f_2$$

$$R_{C_{c2}} = R_E + R_C$$

$$\frac{1}{2\pi R_{C_{c2}} * C_{c2}} \rightarrow f_3$$

$$f_L|_{3dB} = f_1 + f_2 + f_3$$

C_E dominates in the f_L contribution so we make its contribution to 80%.

$$R_{CE} < R_{C_{c1}} \& R_{C_{c2}} \Rightarrow f_{3dB} \text{ contribution by } C_E \text{ is always higher.}$$